

VLSI & Embedded System

MEMORY ELEMENTS


Dennis A. N. Gookyi





CONTENTS



❖ Memory Elements

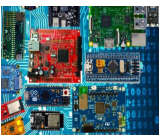



BIG PICTURE: BUILDING A PROCESSOR


❖ Single cycle processor

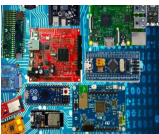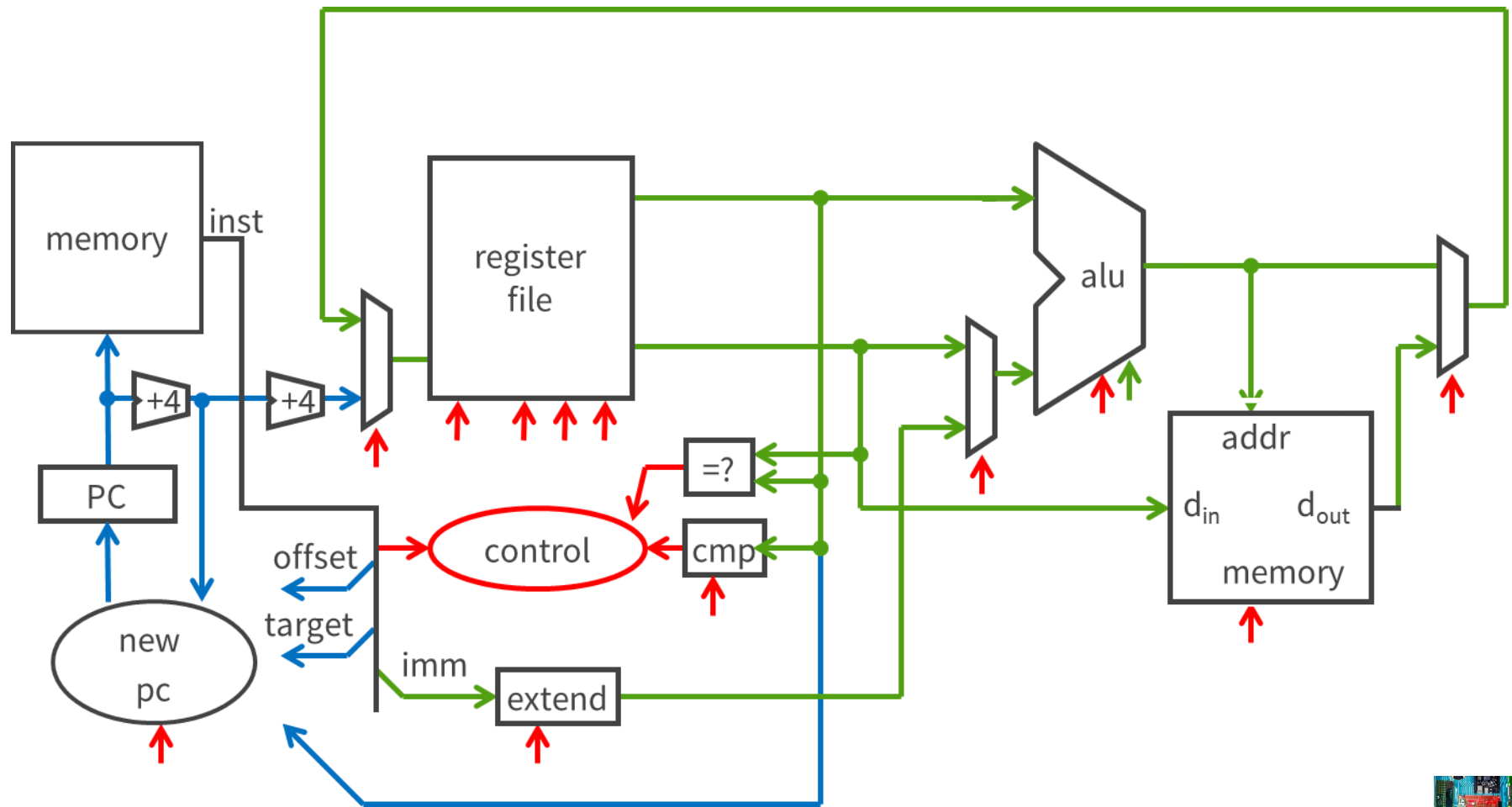




STORING 1-BIT

- ❖ How do we store one bit?

 


STORING 1-BIT

❖ First Attempt: Unstable Devices

 


STORING 1-BIT


❖ First Attempt: Unstable Devices

 

Does not work!


- ☐ Unstable
- ☐ Oscillates wildly!

 

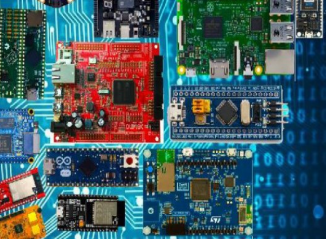



STORING 1-BIT

 - ❖ Second Attempt: Bistable Devices
 - Stable and unstable equilibria



A Simple Device

In stable state, $\bar{A} = B$

  



How do we change the state?



STORING 1-BIT


❖ Third Attempt: Set-Reset Latch

 

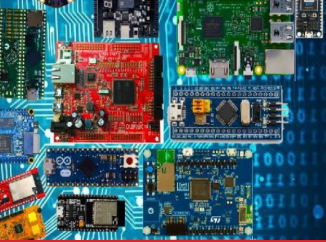

STORING 1-BIT


❖ Third Attempt: Set-Reset Latch

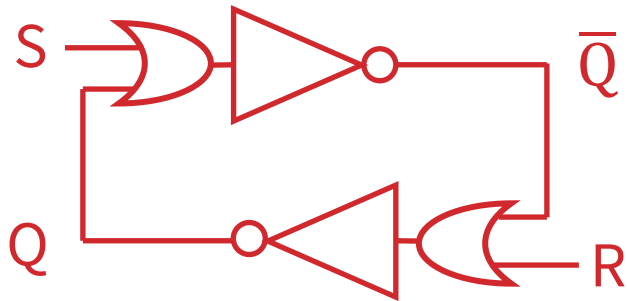


S	R	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0


Set-Reset (S-R) Latch
Stores a value Q and its complement

 

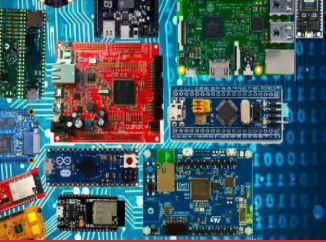

STORING 1-BIT


❖ Third Attempt: Set-Reset Latch

 

S	R	Q	\bar{Q}
0	0		
0	1	0	1
1	0		
1	1		


A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

Set-Reset (S-R) Latch
Stores a value Q and its complement

 

STORING 1-BIT

❖ Third Attempt: Set-Reset Latch

 

S	R	Q	\bar{Q}
0	0		
0	1	0	1
1	0	1	0
1	1		

Set-Reset (S-R) Latch
Stores a value Q and its
complement

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0


What are the values for Q and \bar{Q} ?

- a) 0 and 0
- b) 0 and 1
- c) 1 and 0
- d) 1 and 1



STORING 1-BIT

❖ Third Attempt: Set-Reset Latch

 


If Q is 1, will stay 1
if Q is 0, will stay 0

S	R	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	0	1
1	0	1	0
1	1		

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0


Set-Reset (S-R) Latch
Stores a value Q and its complement



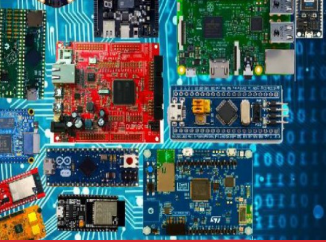

STORING 1-BIT


❖ Third Attempt: Set-Reset Latch

 


S	R	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	0	1
1	0	1	0
1	1	?	?

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0


What happens when S,R changes from 1,1 to 0,0?

 

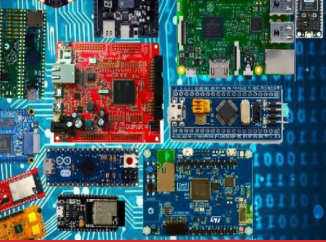

STORING 1-BIT

❖ Third Attempt: Set-Reset Latch

 


S	R	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	0	1
1	0	1	0
1	1	forbidden	

Set-Reset (S-R) Latch
Stores a value **Q** and its complement

What happens when S,R changes from 1,1 to 0,0?



Q and \bar{Q} become unstable and will oscillate wildly between values 0,0 to 1,1 to 0,0 to 1,1 ...

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

 

STORING 1-BIT

❖ Third Attempt: Set-Reset Latch

  


S	R	Q	\bar{Q}	
0	0	Q	\bar{Q}	hold
0	1	0	1	reset
1	0	1	0	set
1	1	forbidden		

Set-Reset (S-R) Latch
Stores a value Q and its complement




STORING 1-BIT

- ❖ Third Attempt: Set-Reset Latch
- ❖ Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit
 - Issue: SR Latch has a forbidden state

 


STORING 1-BIT

❖ Fourth Attempt: (Unclocked) D Latch

 

Fill in the truth table?

 


D	Q	\bar{Q}
0		
1		

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0



STORING 1-BIT

❖ Fourth Attempt: (Unclocked) D Latch

 

Fill in the truth table?


Data (D) Latch

- Easier to use than an SR latch
- No possibility of entering an undefined state

When D changes, Q changes


- ... immediately (...after a delay of 2 Ors and 2 NOTs)

Need to control when the output changes

 

D	Q	\bar{Q}
0	0	1
1	1	0


A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

 




STORING 1-BIT


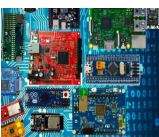
- ❖ Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit
 - Issue: SR Latch has a forbidden state
 - (Unclocked) D Latch can store and change a bit like an SR Latch while avoiding the forbidden state
 - How do we coordinate state changes to a D Latch?




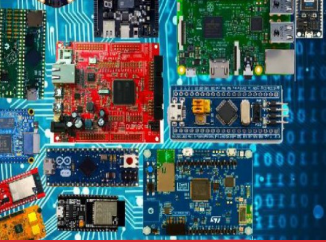

CLOCKS

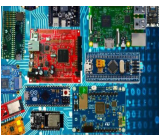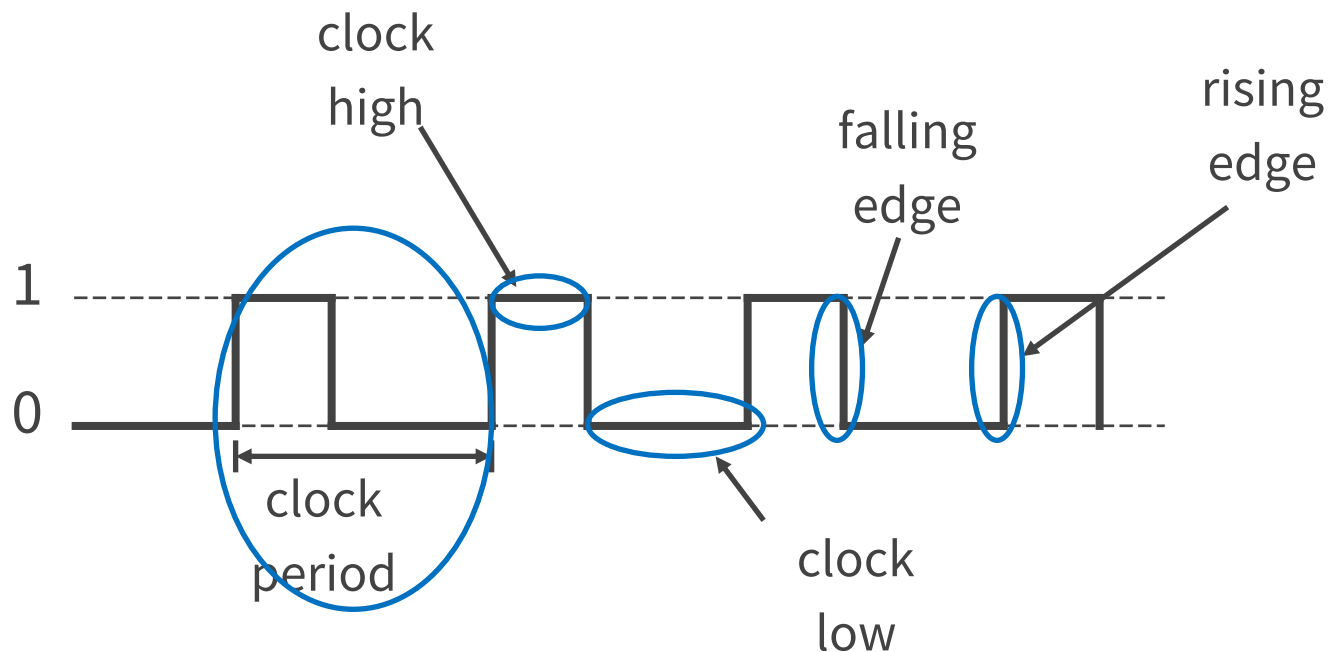- ❖ Clock helps coordinate state changes
 - Usually generated by an oscillating crystal
 - Fixed period
 - Frequency = $1/\text{period}$



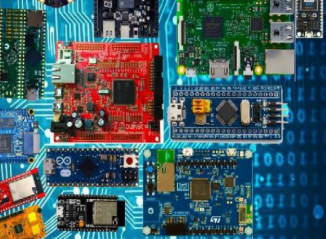

CLOCKS

❖ Clock disciplines

Level sensitive

- State changes when clock is high (or low)




Edge triggered

- State changes at clock edge

positive edge-triggered



negative edge-triggered

 




CLOCKS

❖ Clock Methodology


- Negative edge, synchronous

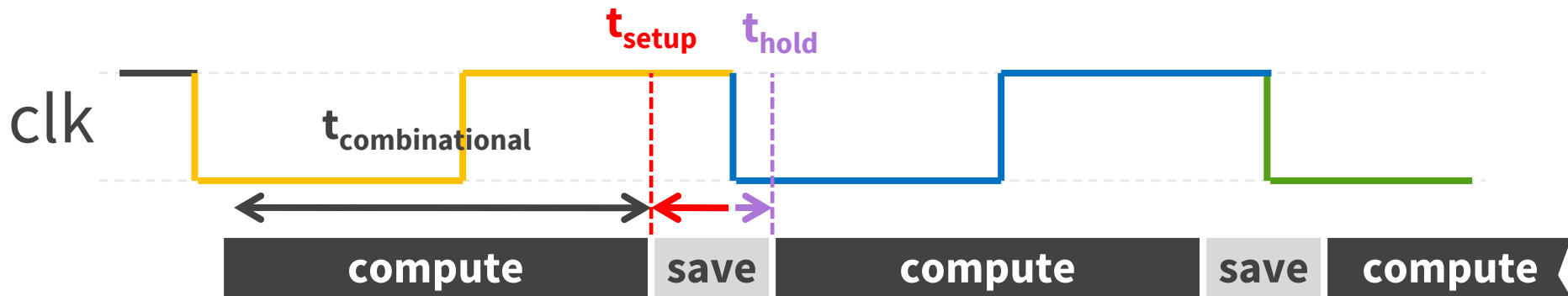


Edge-Triggered → signals must be stable near falling edge

“near” = before and after


t_{setup} t_{hold}

 

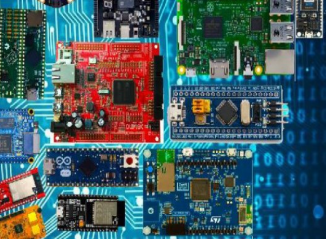


D LATCH

❖ D Latch

 

 - Inverter prevents SR Latch from entering 1,1 state




	D	Q	\bar{Q}
0			
1			

Reset


Set



 


D LATCH

❖ D Latch

 

 - Inverter prevents SR Latch from entering 1,1 state



	D	Q	\bar{Q}
	0	0	1
	1	1	0


Reset

Set






D LATCH

 

$C = 1$, D Latch *transparent*:
set/reset (according to D)

$C = 0$, D Latch *opaque*:
keep state (ignore D)

 - Level sensitive
- Inverter prevents SR Latch from entering 1,1 state
- C enables changes



C	D	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		

No
Change


Reset

Set






D LATCH

 

$C = 1$, D Latch *transparent*:
set/reset (according to D)

$C = 0$, D Latch *opaque*:
keep state (ignore D)

S	R	Q	\bar{Q}	
0	0	Q	\bar{Q}	hold
0	1	0	1	reset
1	0	1	0	set
1	1	forbidden		

 


- Level sensitive
- Inverter prevents SR Latch from entering 1,1 state
- C enables changes

C	D	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	Q	\bar{Q}
1	0	0	1
1	1	1	0

Reset


Set



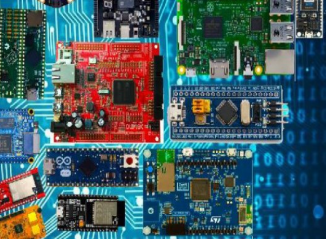


D LATCH

❖ D Latch

 

What is the value of Q at A & B?

 - a) $A = 0, B = 0$
- b) $A = 0, B = 1$
- c) $A = 1, B = 0$
- d) $A = 1, B = 1$




clk	D	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	Q	\bar{Q}
1	0	0	1
1	1	1	0





D LATCH

❖ D Latch

 


What is the value of Q at A & B?

a) $A = 0, B = 0$

b) $A = 0, B = 1$


c) $A = 1, B = 0$

d) $A = 1, B = 1$

 


clk	D	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	Q	\bar{Q}
1	0	0	1
1	1	1	0



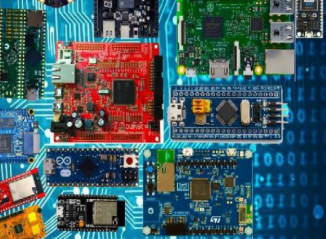

D LATCH

❖ D Latch

 


Level Sensitive D Latch

Clock high:

set/reset (according to D)


Clock low:

keep state (ignore D)

 


clk	D	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	Q	\bar{Q}
1	0	0	1
1	1	1	0



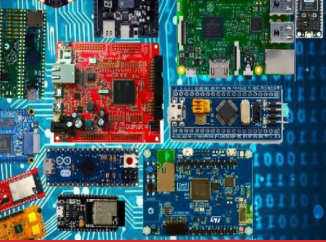

D FLIP-FLOP


❖ D flip-flop

 


- **Edge-Triggered**
- **Data captured when the clock is high**
- **Output changes only on falling edges**

❖ Master-Slave Flip Flop

 - Outputs change only on falling edges
- Data is captured on rising edges
- ❖ 1 cycle delay but works out perfectly – data for the next stage is ready 1 cycle ahead of time



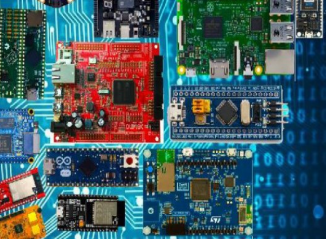


D FLIP-FLOP

❖ D flip-flop

Clock = 1: L1 transparent
L2 opaque

 
When CLK rises ($0 \rightarrow 1$),
now X can change,
Q does not change




Clock = 0: L1 opaque
L2 transparent

When **CLK falls** ($1 \rightarrow 0$),


Q gets X, X cannot change

 

 

D FLIP-FLOP

What is the value of Q at A & B?

 


a) $A = 0, B = 0$

b) $A = 0, B = 1$

c) $A = 1, B = 0$


d) $A = 1, B = 1$

 



D FLIP-FLOP

What is the value of Q at A & B?

 


a) $A = 0, B = 0$

b) $A = 0, B = 1$

c) $A = 1, B = 0$


d) $A = 1, B = 1$

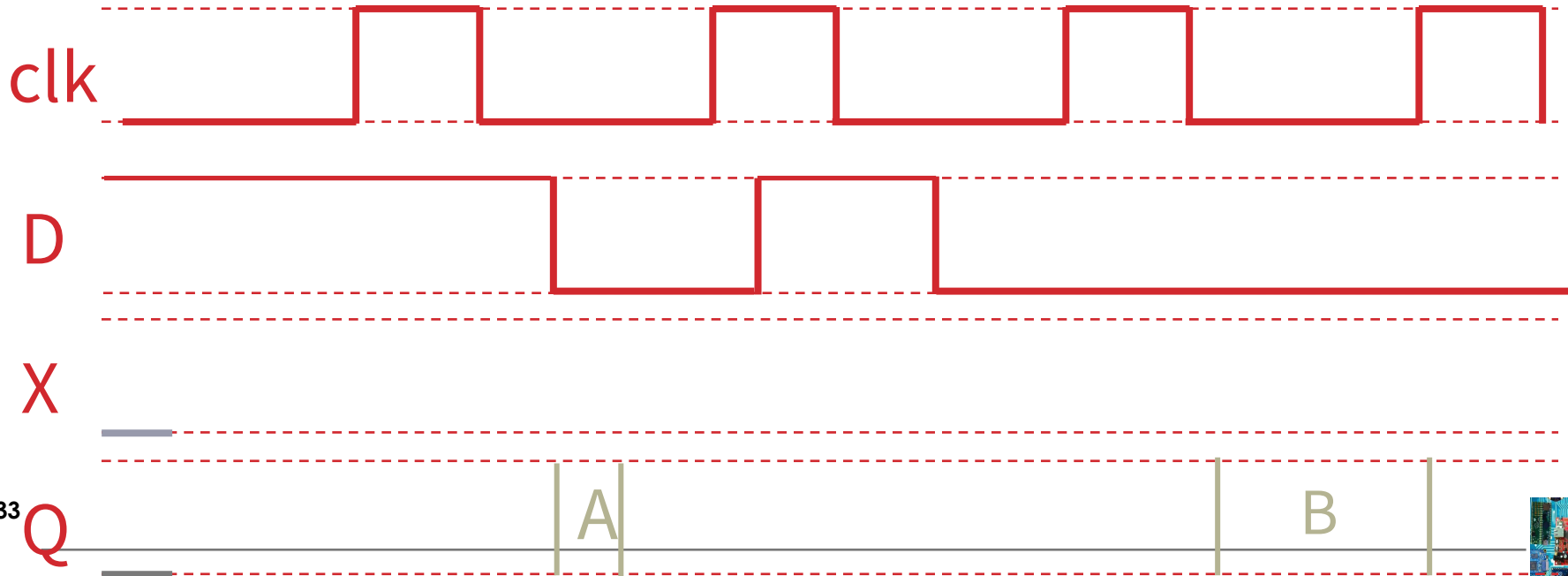




D FLIP-FLOP

- ❖ Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit
 - SR Latch has a forbidden state
- ❖ (Unclocked) D Latch can store and change a bit like an SR Latch while avoiding a forbidden state
- ❖ An Edge-Triggered D Flip-Flop (aka Master-Slave D Flip-Flop) stores one bit
 - The bit can be changed in a synchronized fashion on the edge of a clock signal
- ❖ How do we store more than one bit, N bits?

 


STORING MORE BITS

❖ Registers

 


 - D flip-flops in parallel
- shared clock
- extra clocked inputs: write_enable, reset, ...





STORING MORE BITS

❖ Registers

 


 
- D flip-flops in parallel
- shared clock
- extra clocked inputs: write_enable, reset, ...



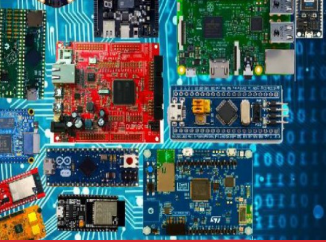

BIG PICTURE: BUILDING A PROCESSOR


❖ Single cycle processor

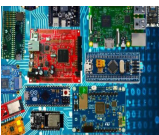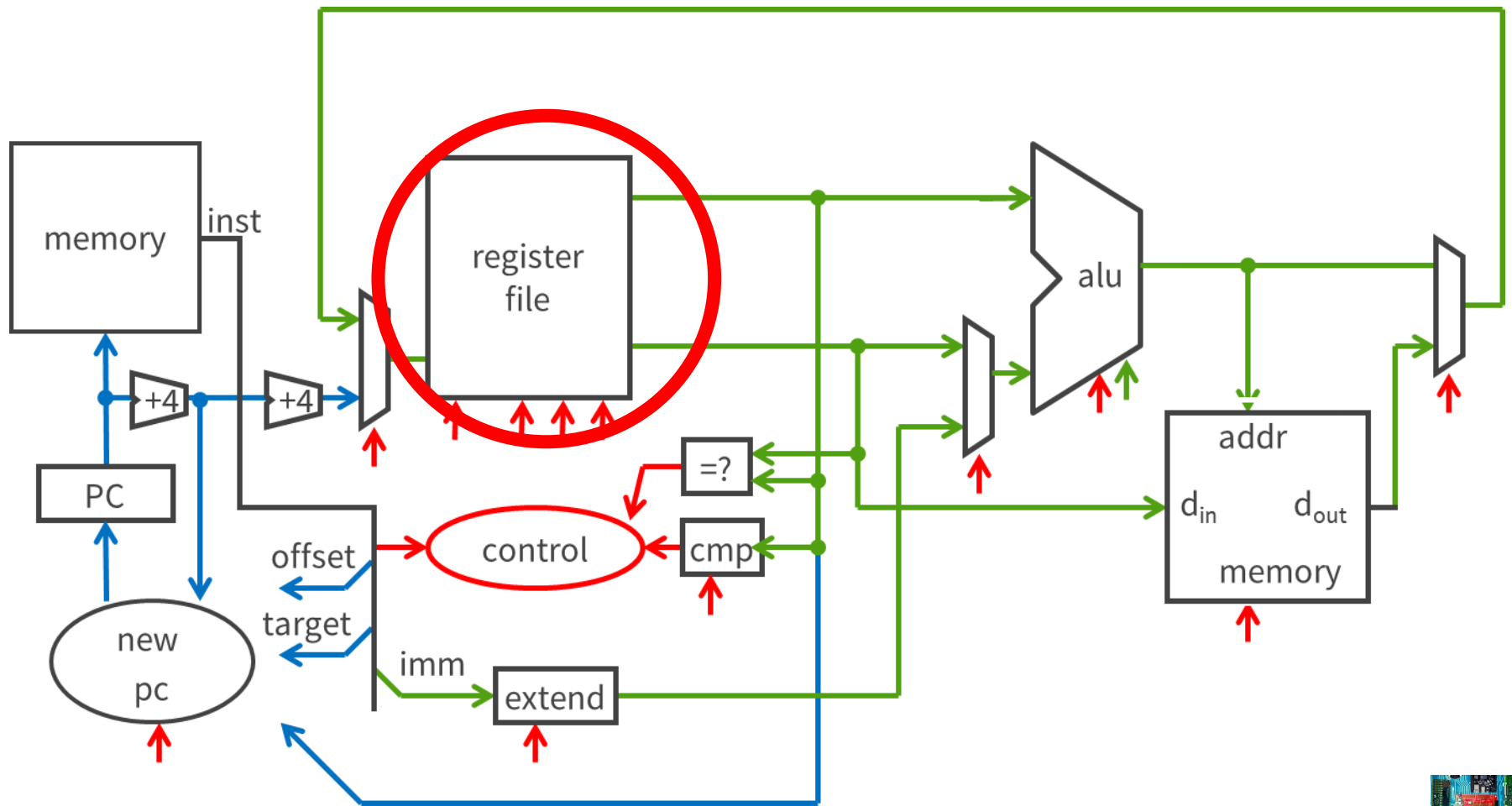

REGISTER FILE

❖ Register file

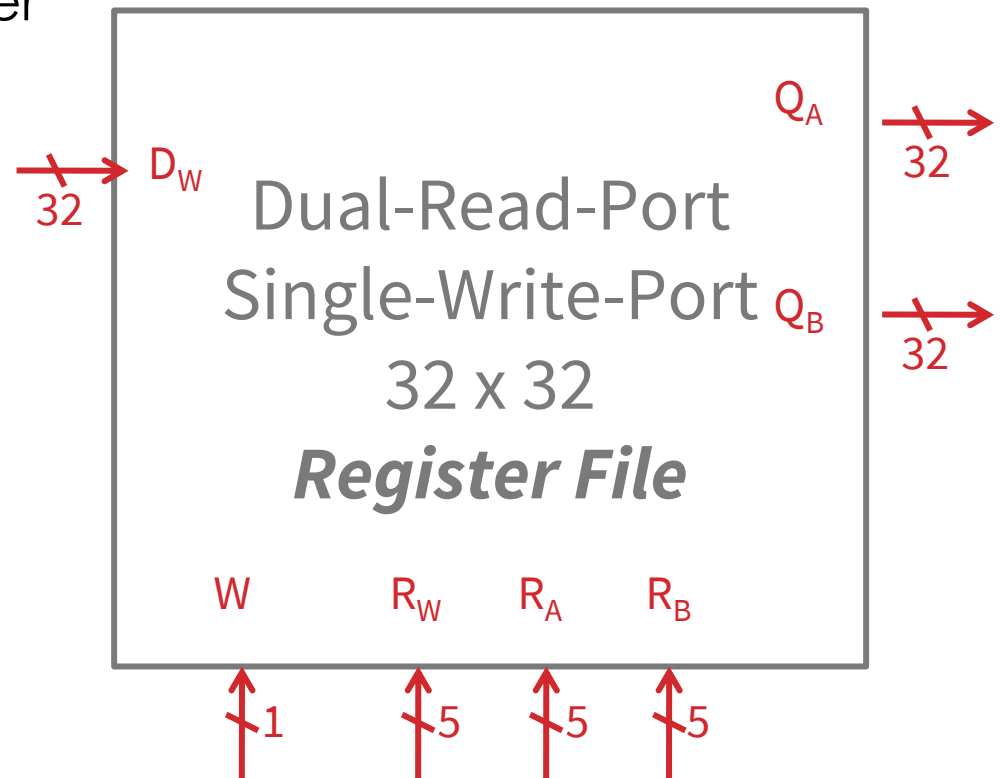- N read/write registers
- Indexed by register number




REGISTER FILE

❖ Register file

- N read/write registers
- Indexed by register number

`addi x1, x0, 10`

 

❖ How to write one register in the register file



- Need a decoder




REGISTER FILE

❖ 3-to-8 decoder truth table and circuit

i2	i1	i0	o0	o1	o2	o3	o4	o5	o6	o7
0	0	0								
0	0	1								
0	1	0								
0	1	1								
1	0	0								
1	0	1								
1	1	0								
1	1	1								

  


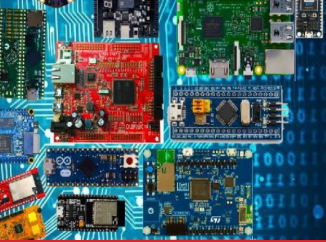




REGISTER FILE

❖ 3-to-8 decoder truth table and circuit

i2	i1	i0	o0	o1	o2	o3	o4	o5	o6	o7
0	0	0	1							
0	0	1		1						
0	1	0			1					
0	1	1				1				
1	0	0					1			
1	0	1						1		
1	1	0							1	
1	1	1								1

 

3 R_W 001

   

REGISTER FILE


❖ Register file

- N read/write registers
- Indexed by register number

add x1, x0, x5

How to read from two registers?

- Need a multiplexor

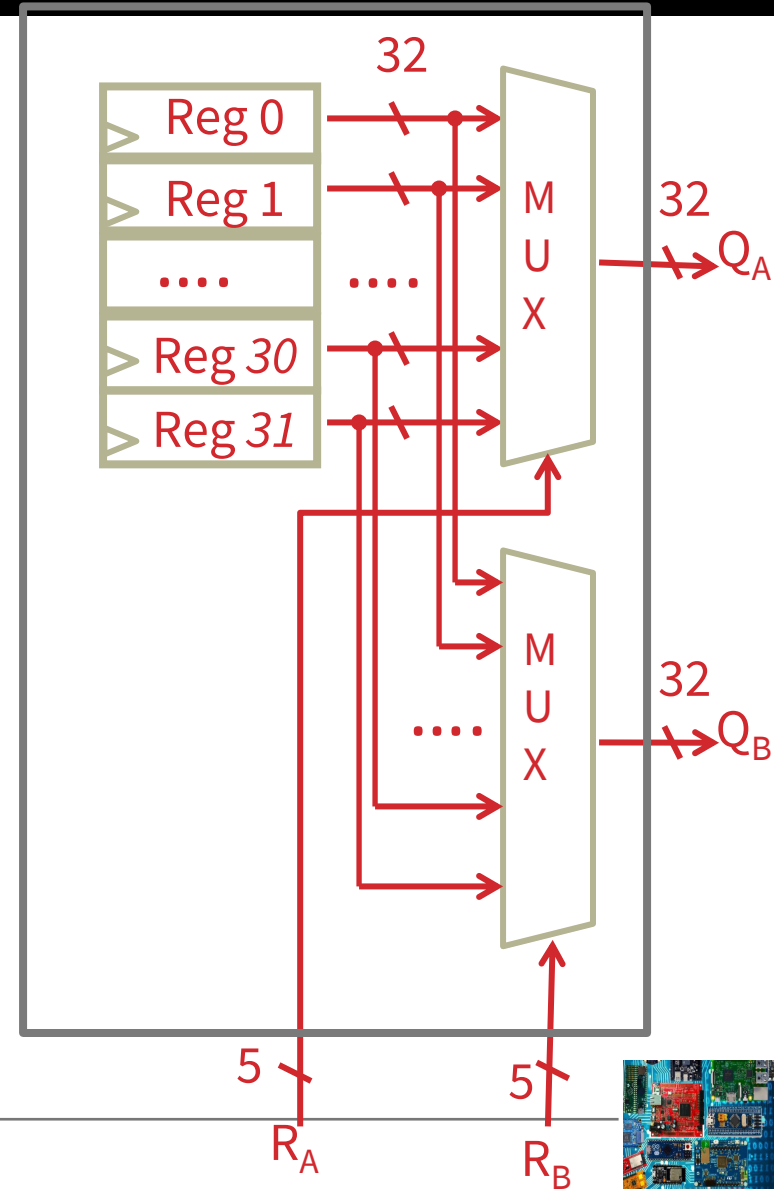


REGISTER FILE

❖ Register file

- N read/write registers
- Indexed by register number

❖ Implementation:

 - D flip flops to store bits
- Decoder for each write port
- Mux for each read port






REGISTER FILE

❖ Register file

- ❑ N read/write registers
- ❑ Indexed by register number

❖ Implementation:

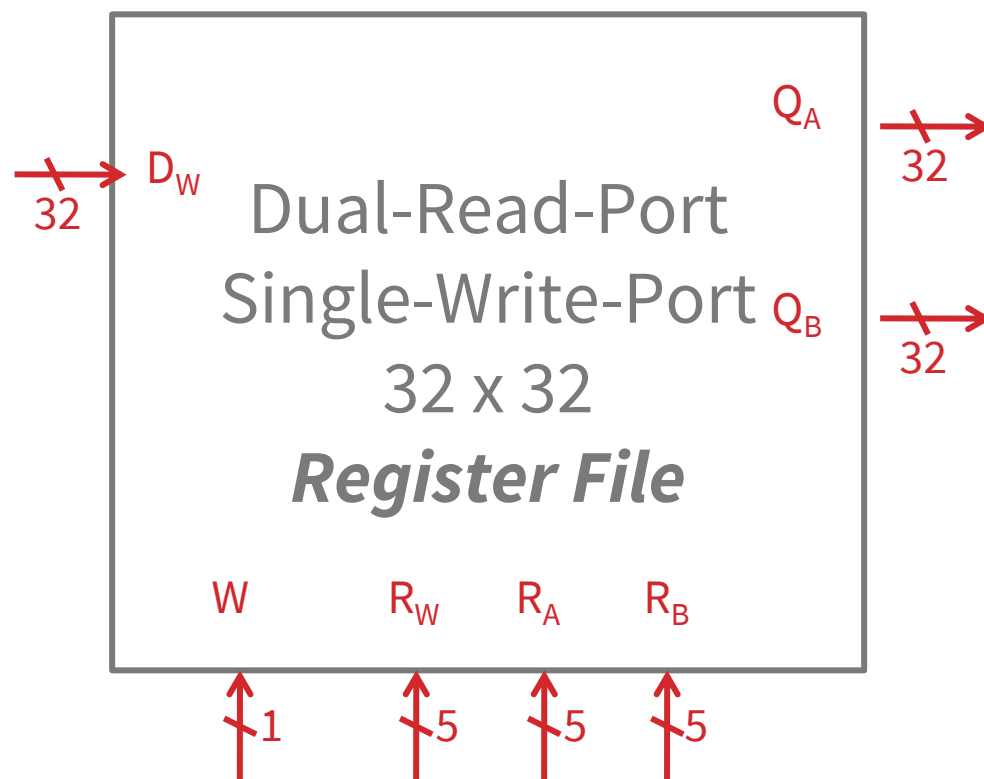
- ❑ D flip flops to store bits
- ❑ Decoder for each write port
- ❑ Mux for each read port



REGISTER FILE

❖ Register file

 
- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward
- Doesn't scale
e.g. 32Mb register file with 32 bit registers
Need 32x 1M-to-1 multiplexor and 32x 20-to-1M decoder
How many logic gates/transistors?





BIG PICTURE: BUILDING A PROCESSOR



❖ Single cycle processor

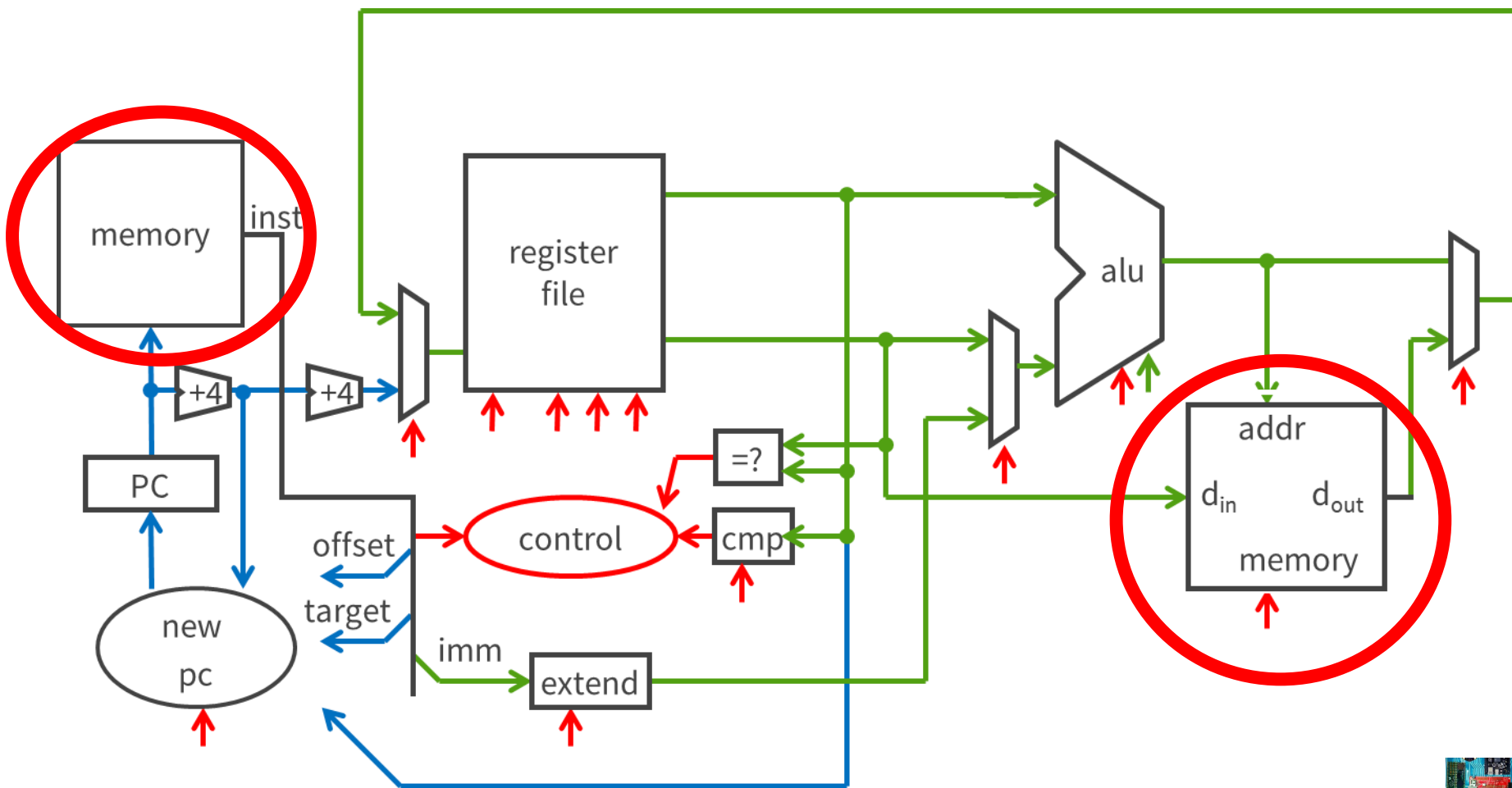




BUILDING LARGE MEMORIES

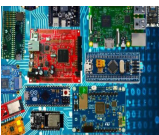 - ❖ Need a shared bus (or shared bit line)
 - Many FlipFlops/outputs/etc. connected to single wire
 - Only one output drives the bus at a time




 

BUILDING LARGE MEMORIES

❖ Tri-State Buffers

 - If enabled ($E=1$), then $Q = D$
- Otherwise, Q is not connected (z = high impedance)



E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1







BUILDING LARGE MEMORIES

❖ Tri-State Buffers

 - If enabled ($E=1$), then $Q = D$
- Otherwise, Q is not connected (z = high impedance)



E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

 





BUILDING LARGE MEMORIES


❖ Tri-State Buffers

 - If enabled ($E=1$), then $Q = D$
- Otherwise, Q is not connected (z = high impedance)



E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

 


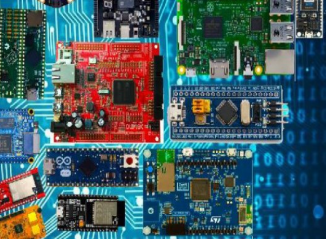

BUILDING LARGE MEMORIES

❖ Tri-State Buffers

 
- If enabled ($E=1$), then $Q = D$
- Otherwise, Q is not connected (z = high impedance)



E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

A	B	AND	NAND
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

 




BUILDING LARGE MEMORIES

❖ Tri-State Buffers

 
- If enabled ($E=1$), then $Q = D$
- Otherwise, Q is not connected (z = high impedance)




E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

A	B	AND	NAND
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

 


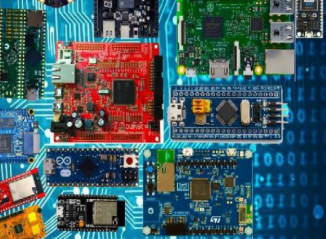

BUILDING LARGE MEMORIES

❖ Tri-State Buffers

 
- If enabled ($E=1$), then $Q = D$
- Otherwise, Q is not connected (z = high impedance)



E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

A	B	AND	NAND
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0


A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

 





BUILDING LARGE MEMORIES

❖ Shared bus

 

 
- ❖ Tri-state Buffers allow scaling since multiple registers can be connected to a single output, while only one register actually drives the output



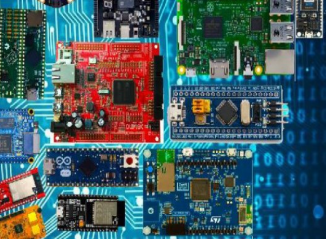

MEMORY

 - ❖ Storage Cells + bus
- ❖ Inputs: Address, Data (for writes)
- ❖ Outputs: Data (for reads)
- ❖ Also need R/W signal (not shown)



- ❖ N address bits $\rightarrow 2^N$ words total
- ❖ M data bits \rightarrow each word M bits


- ❖ How many address bits are necessary for a 4M x 8 SRAM module?
 - 4M word lines that are each 8 bits wide





MEMORY

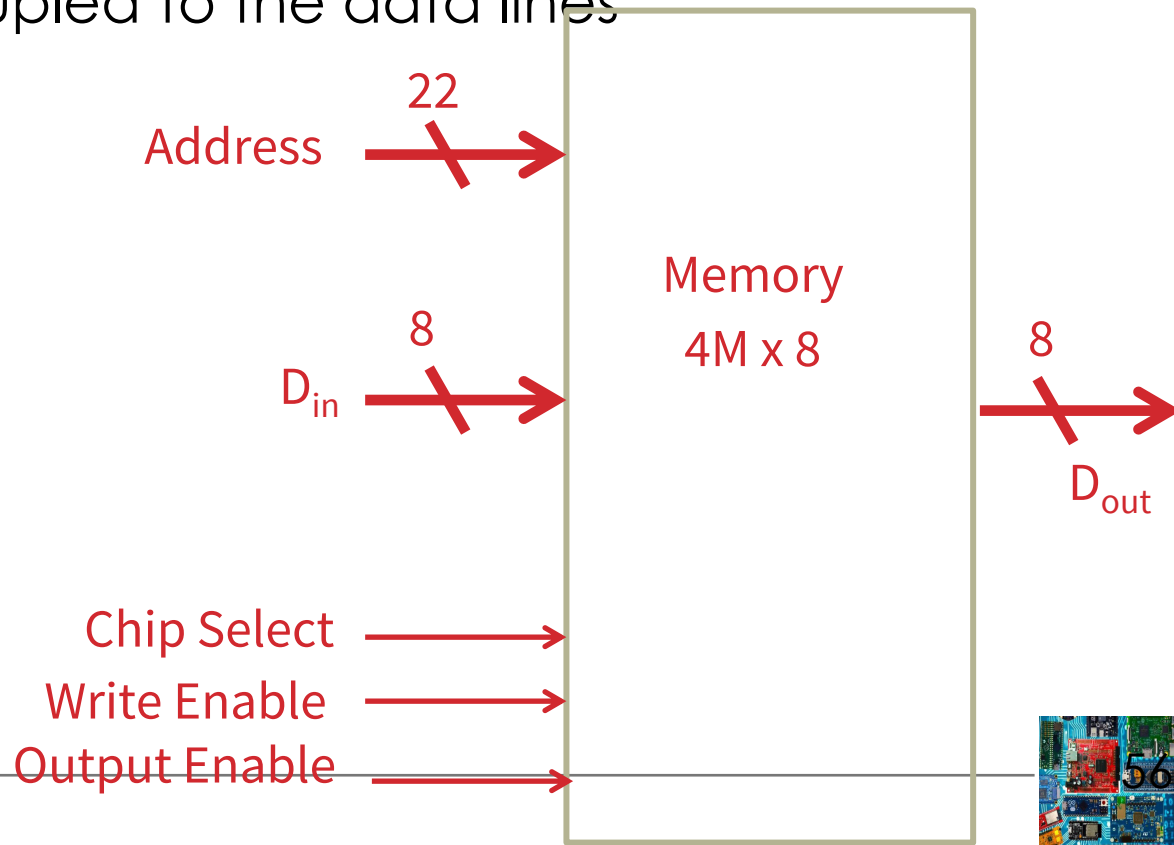- ❖ Storage Cells + bus
- ❖ Decoder selects a word line
- ❖ R/W selector determines access type
- ❖ Word line is then coupled to the data lines







MEMORY

❖ How do we design a 4 x 2 Memory Module?


- 4 word lines that are each 2 bits wide

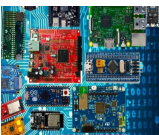 

MEMORY

❖ How do we design a 4 x 2 Memory Module?

□ 4 word lines that are each 2 bits wide


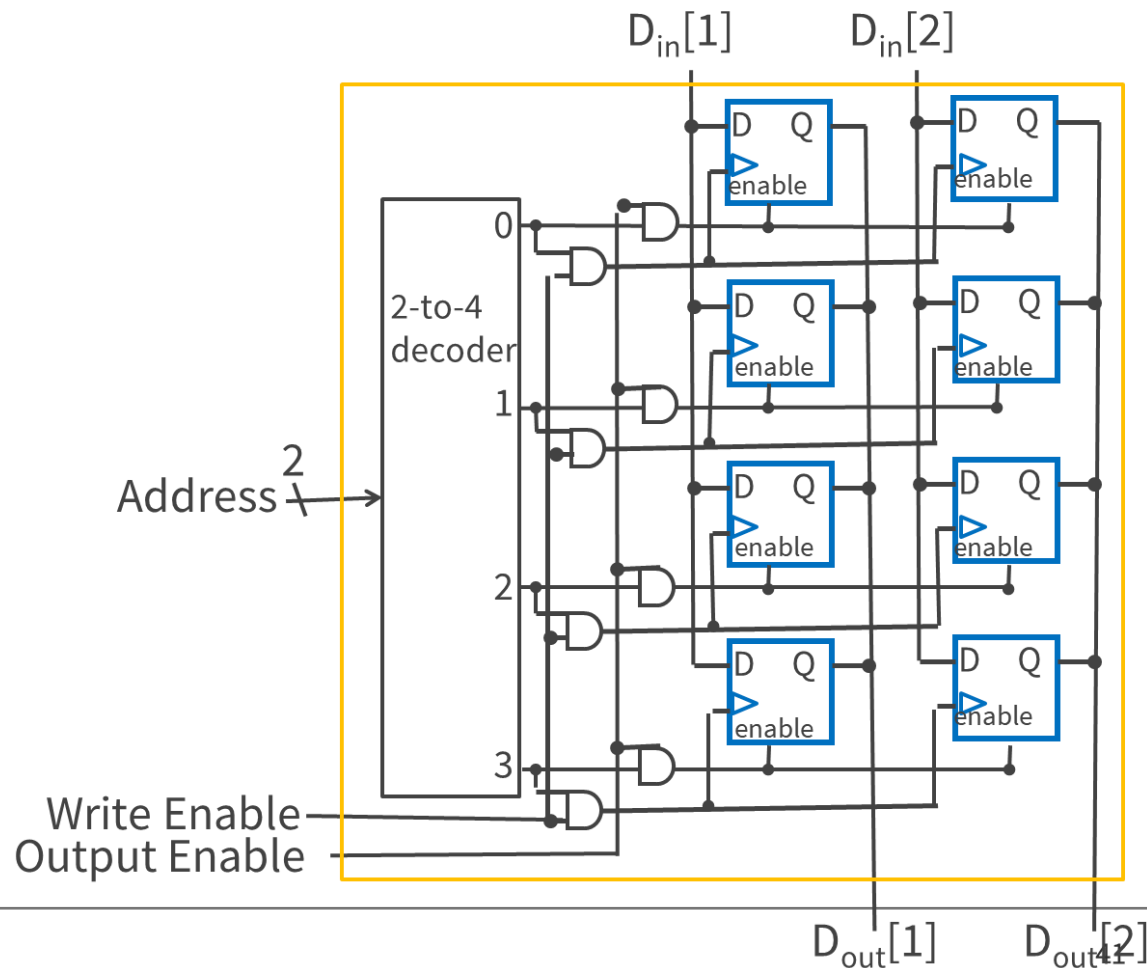




MEMORY

❖ How do we design a 4 x 2 Memory Module?



- 4 word lines that are each 2 bits wide

  

MEMORY

❖ How do we design a 4 x 2 Memory Module?

- 4 word lines that are each 2 bits wide

 
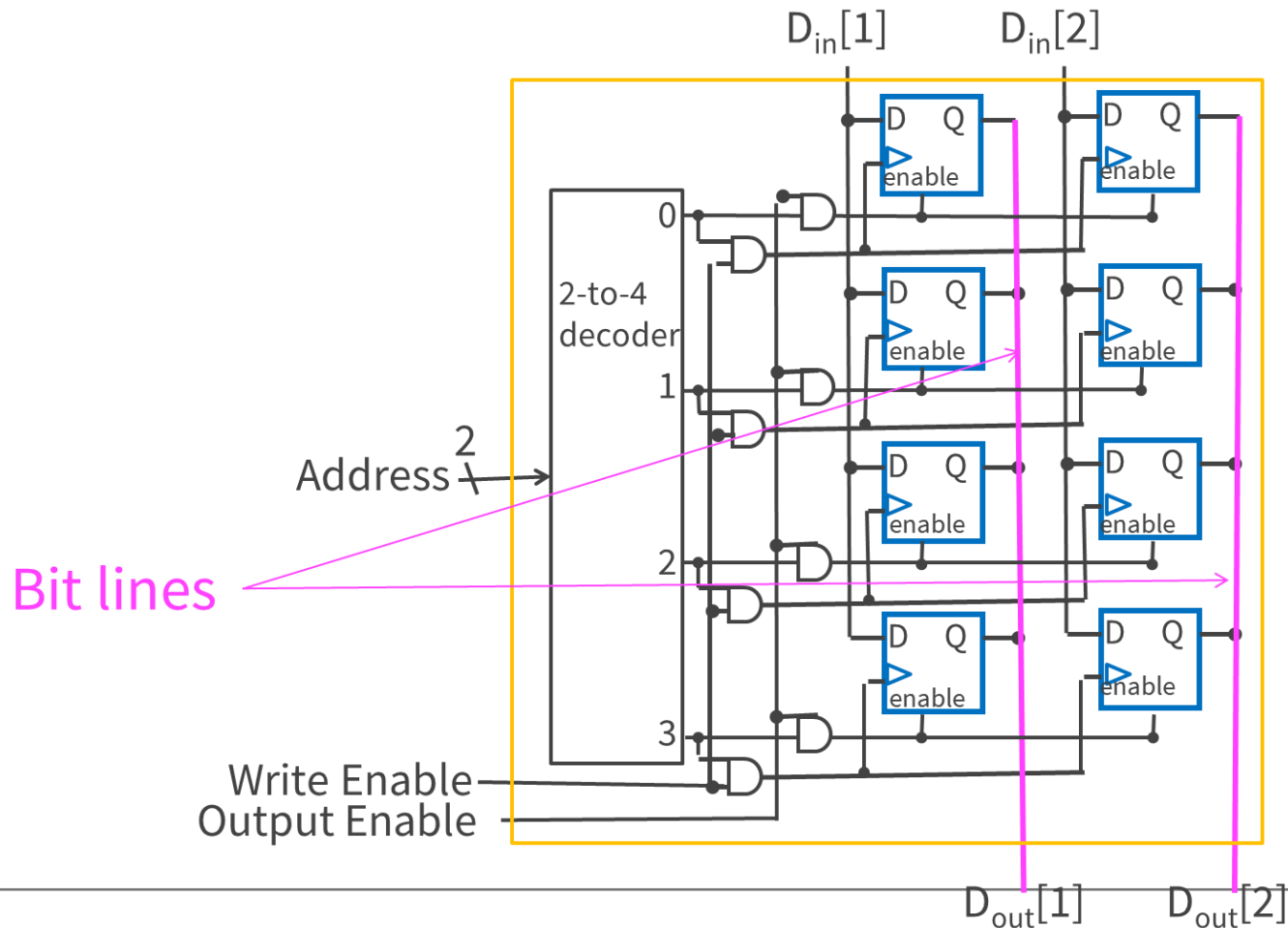




SRAM CELL

❖ Typical SRAM cell

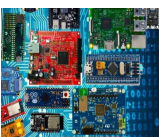 
- Each cell stores one bit, and requires 4 – 8 transistors (6 is typical)





SRAM CELL

❖ Typical SRAM cell

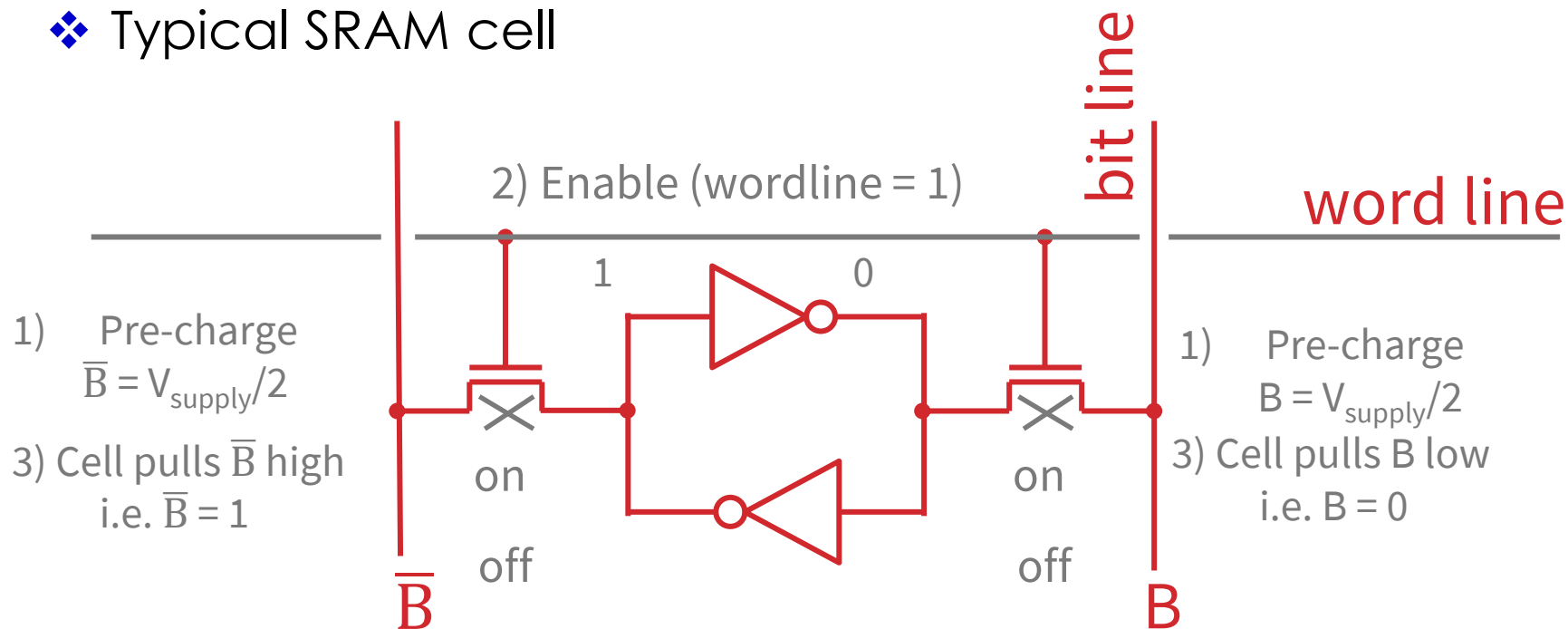

Each cell stores one bit, and requires 4 – 8 transistors (6 is typical)

Read:

- pre-charge B and \bar{B} to $V_{\text{supply}}/2$
- pull word line high
- cell pulls B or \bar{B} low, sense amp detects voltage difference





bit line



Read:



- Write:

- pull word line high
- drive B and \bar{B} to flip cell

MEMORY

❖ How do we design a 4 x 2 Memory Module?


- 4 word lines that are each 2 bits wide

 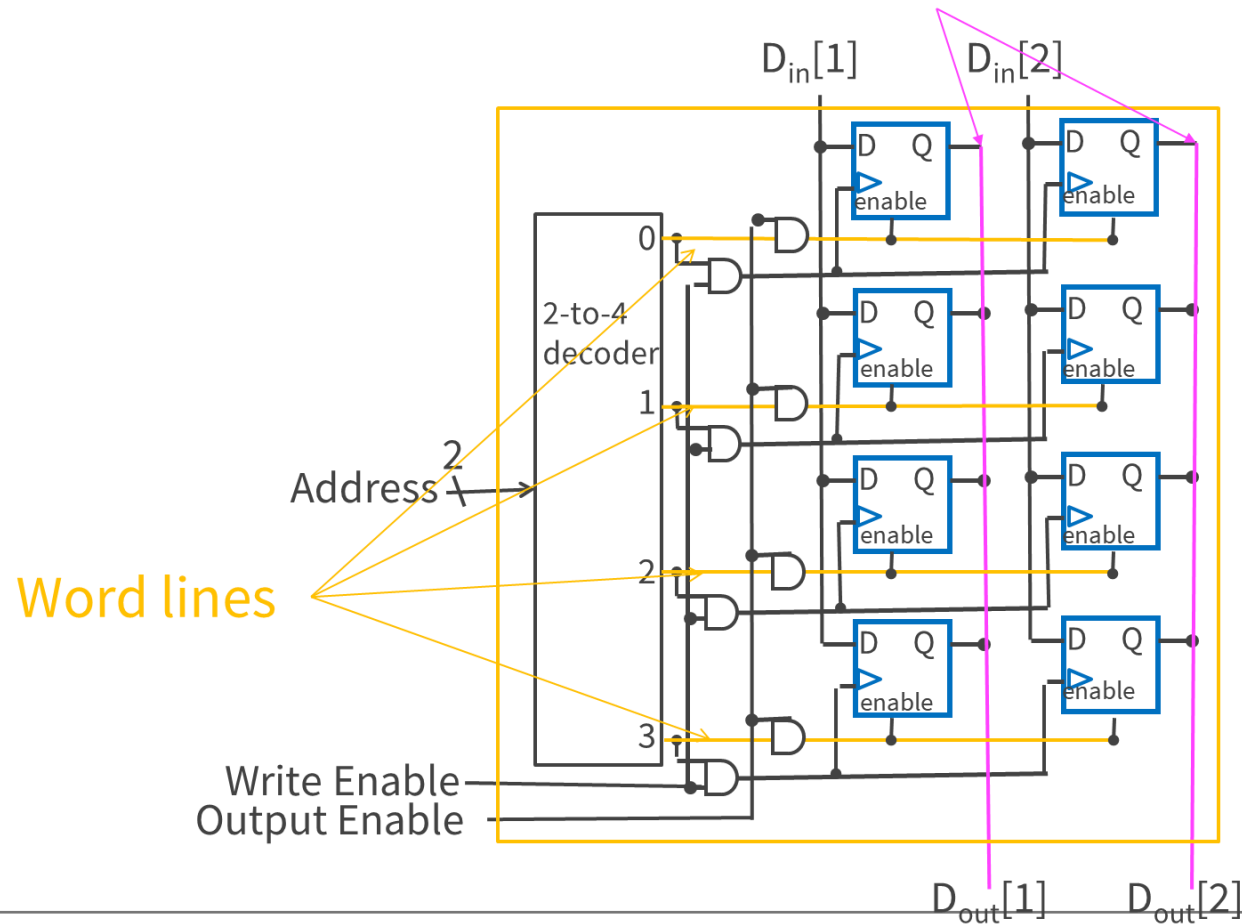

MEMORY

❖ How do we design a 4M x 8 Memory Module?

 □ 4M word lines that are each 8 bits wide $D_{in} \downarrow 8$






MEMORY

❖ How do we design a 4M x 8 Memory Module?

- 4M word lines that are each 8 bits wide

4M x 8 SRAM

 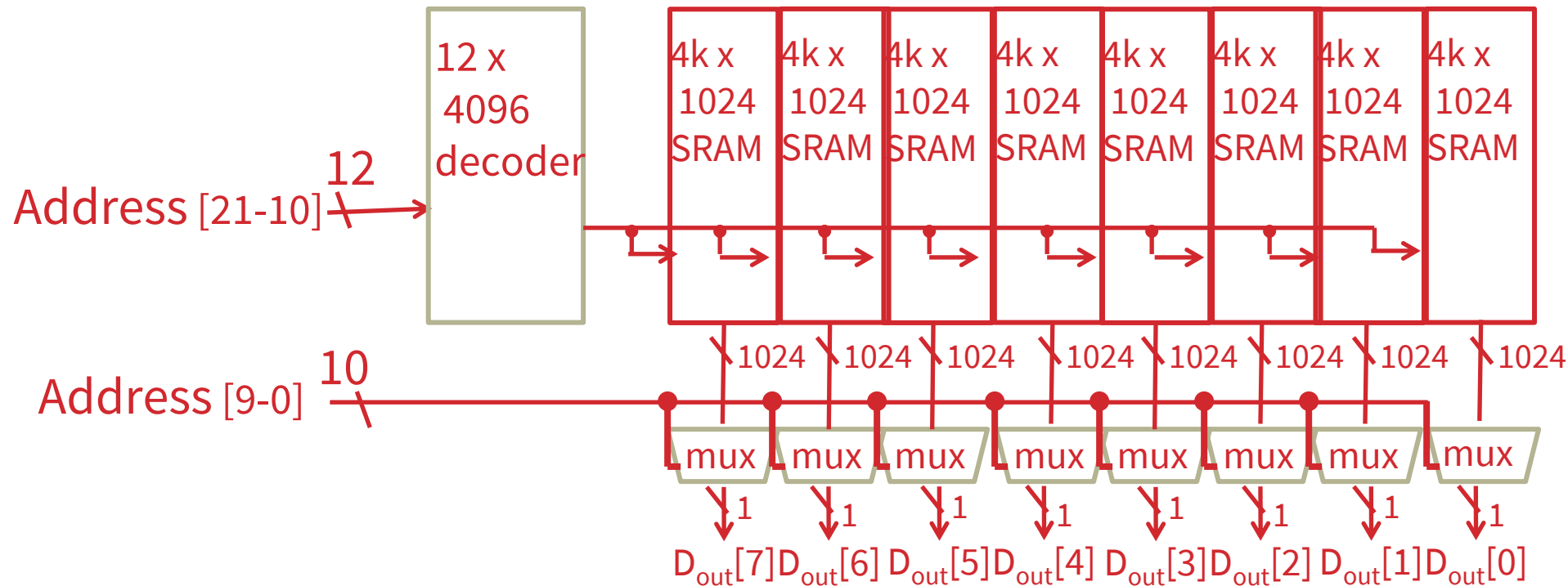


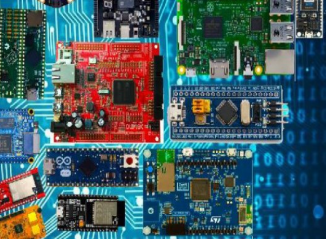

MEMORY

❖ How do we design a 4M x 8 Memory Module?

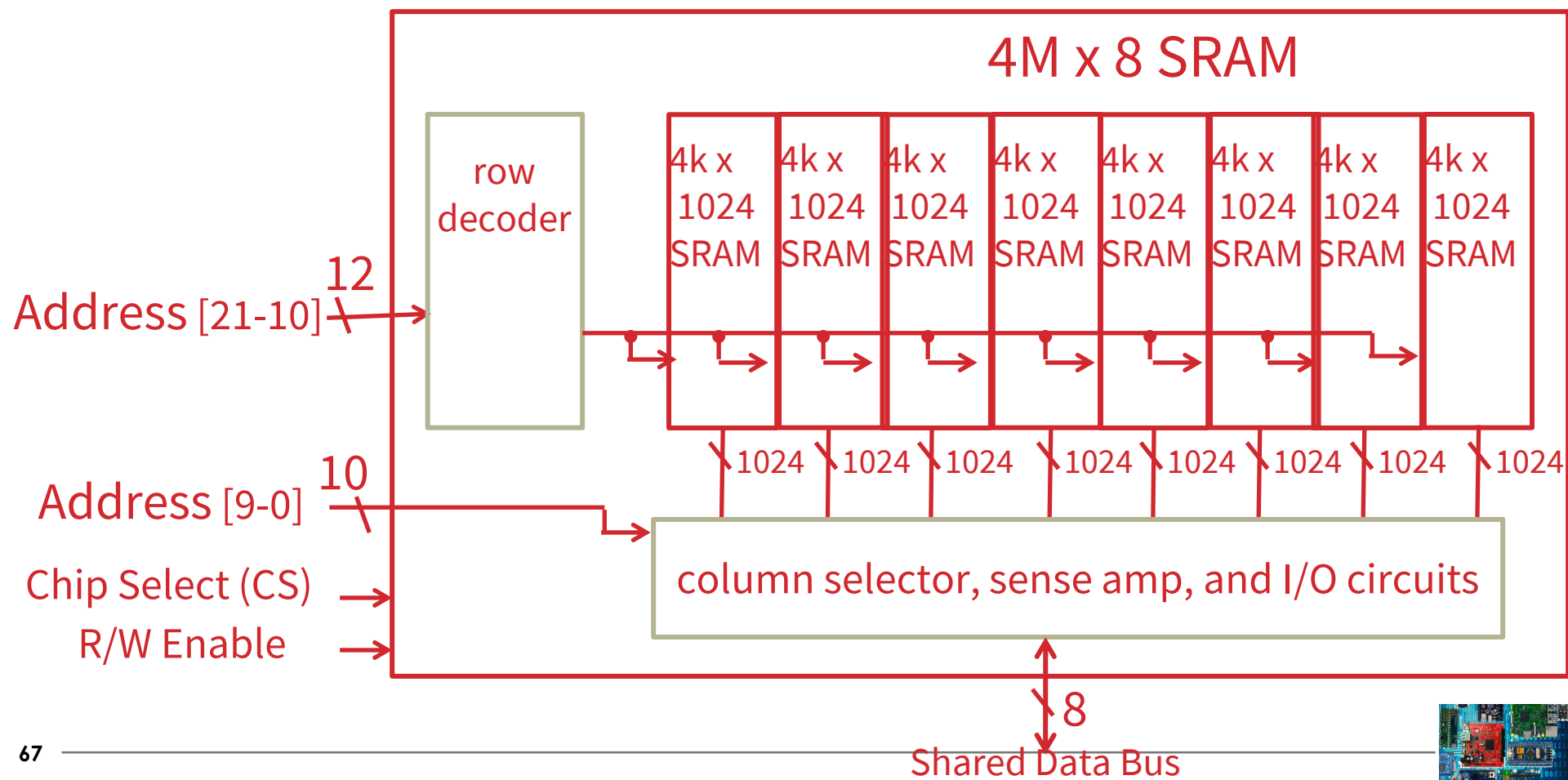- 4M word lines that are each 8 bits wide







MEMORY



SRAM modules arrays

 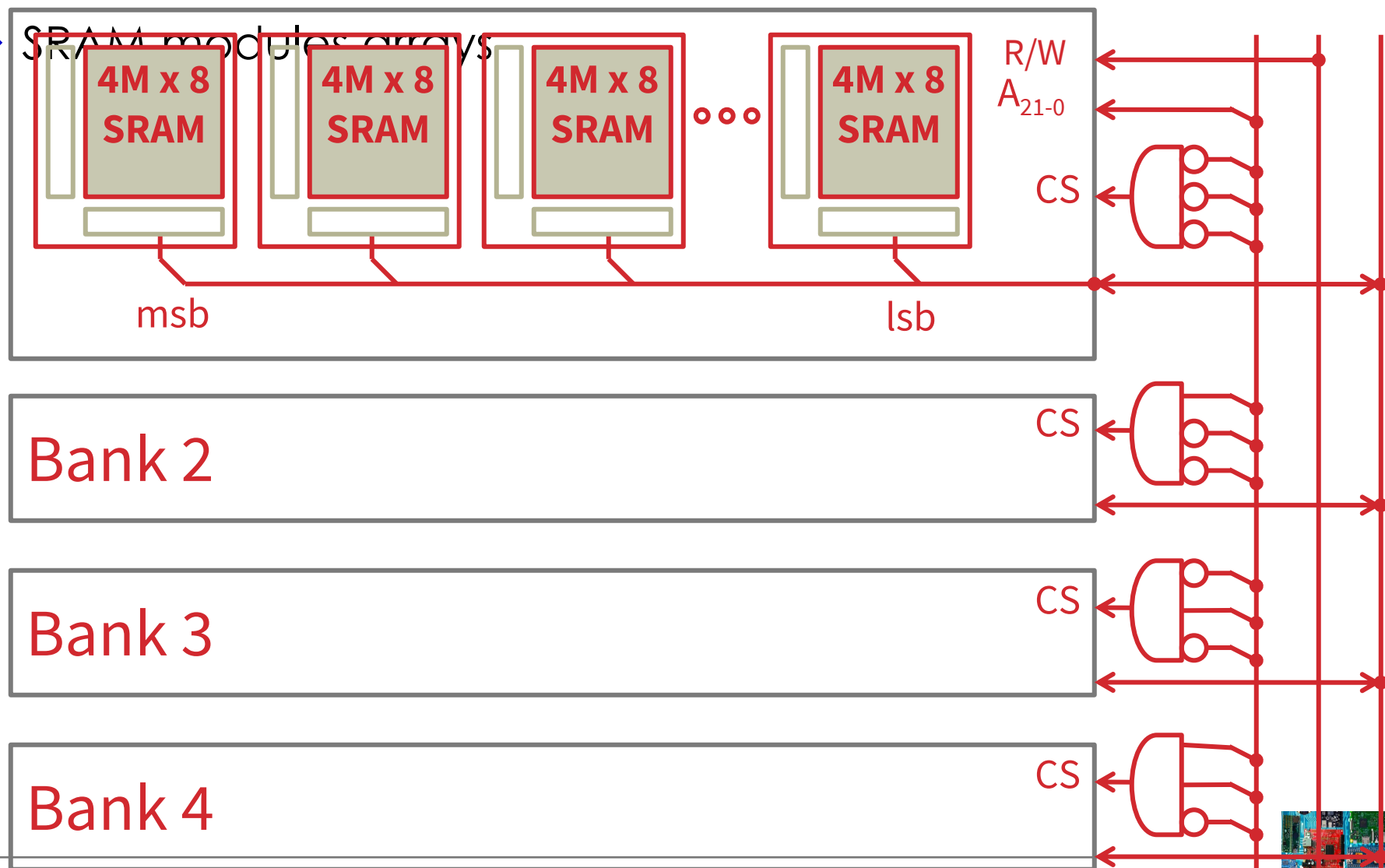





MEMORY

❖ Dynamic-RAM (DRAM)

- Data values require constant refresh

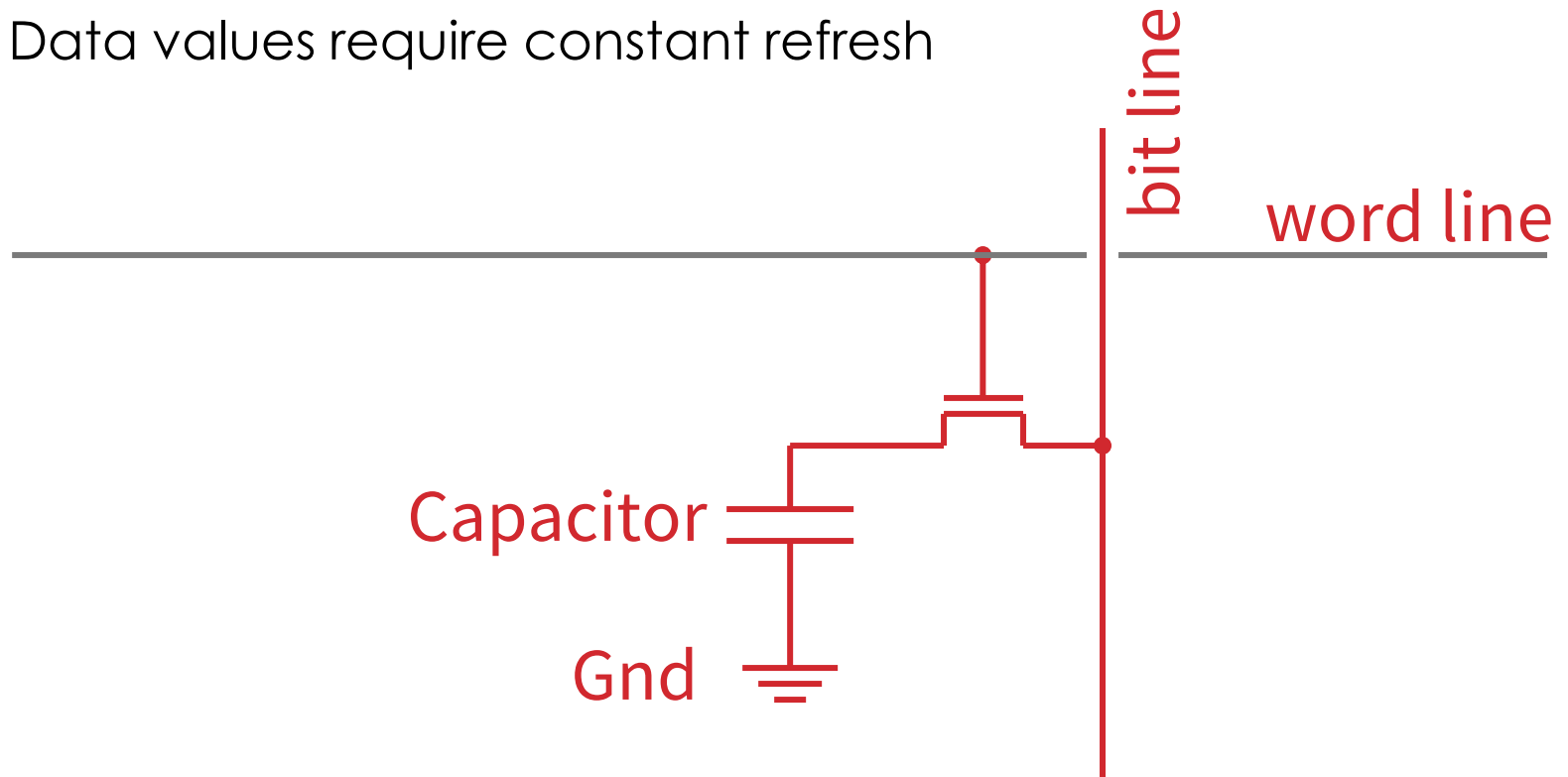

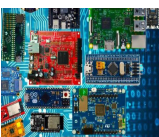Each cell stores one bit, and requires 1 transistors






MEMORY


❖ Dynamic-RAM (DRAM)

- Data values require constant refresh

 

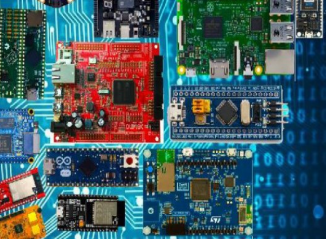Each cell stores one bit, and requires 1 transistors






MEMORY


❖ Dynamic-RAM (DRAM)

- Data values require constant refresh

 

 
Each cell stores one bit, and requires 1 transistors





MEMORY

❖ Dynamic RAM (DRAM)

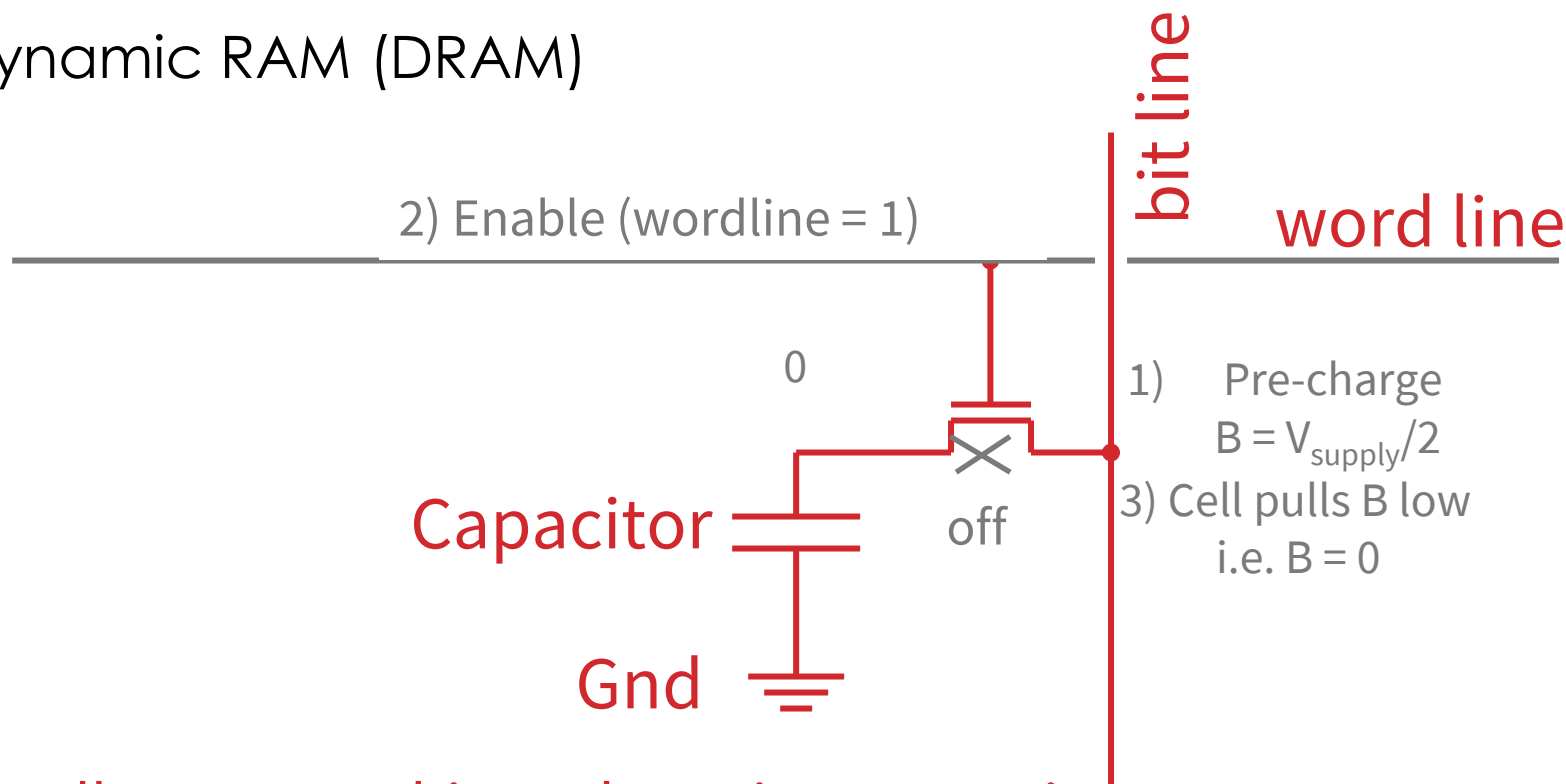

Each cell stores one bit, and requires 1 transistors

Read:

- pre-charge B and \bar{B} to $V_{\text{supply}}/2$
- pull word line high
- cell pulls B low, sense amp detects voltage difference






MEMORY

❖ Dynamic RAM (DRAM)

1) Enable (wordline = 1)

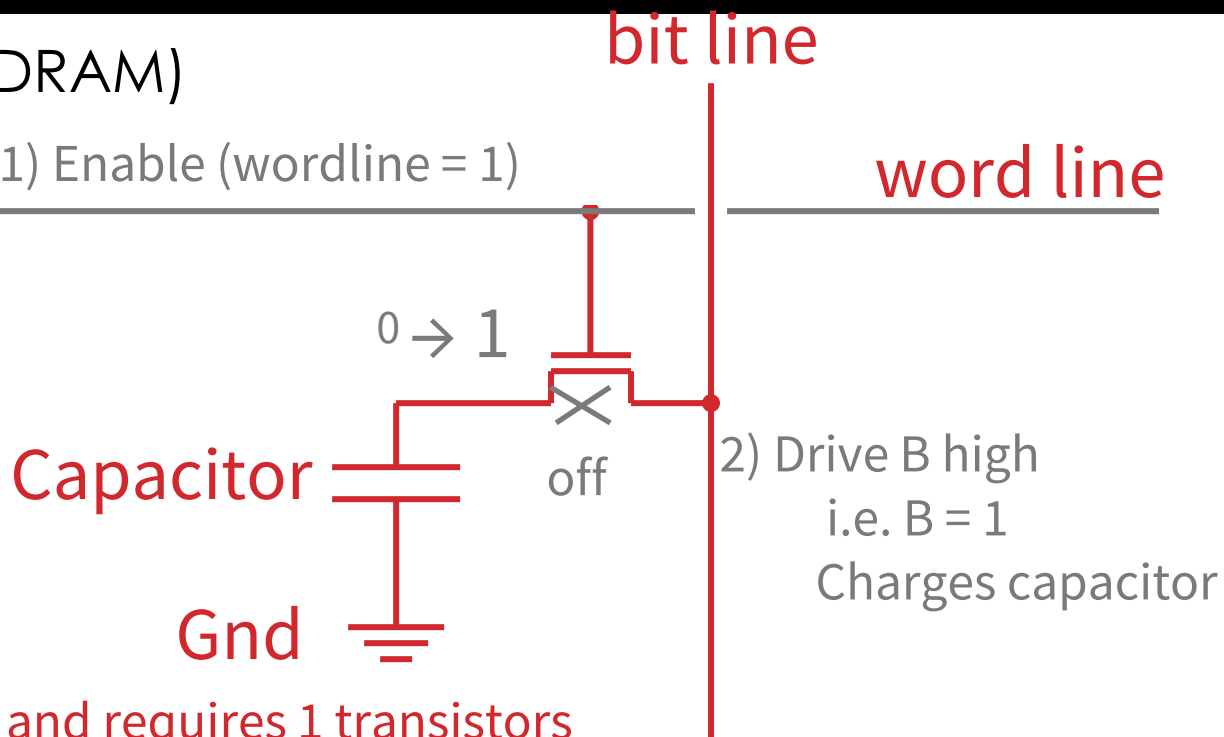

Each cell stores one bit, and requires 1 transistors

Read:

- pre-charge B and \bar{B} to $V_{\text{supply}}/2$
- pull word line high
- cell pulls B low, sense amp detects voltage difference

Write:

- pull word line high
- drive B charges capacitor






MEMORY


❖ Dynamic-RAM (DRAM)

- Data values require constant refresh

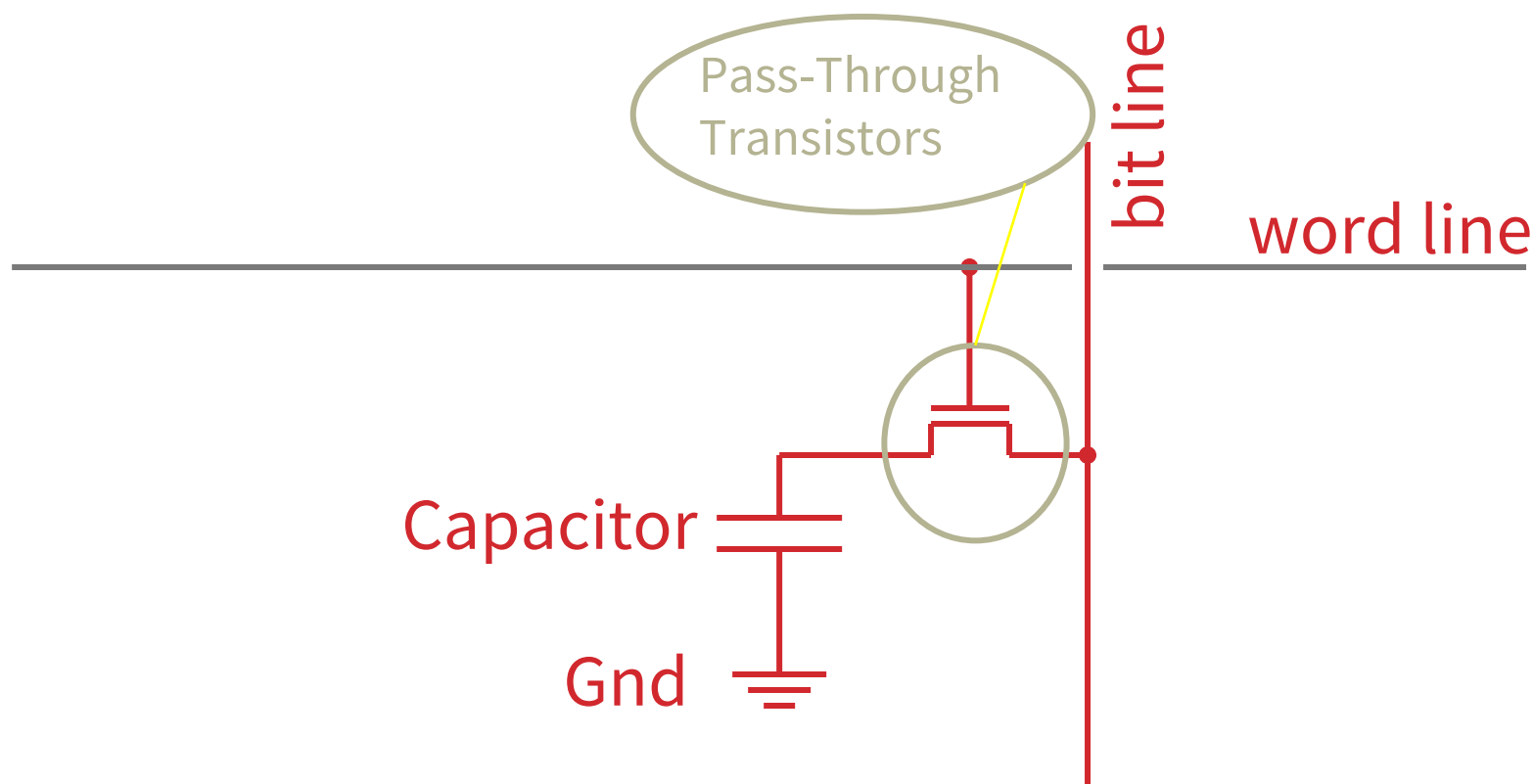

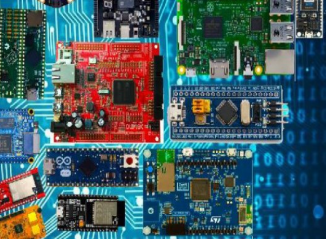Each cell stores one bit, and requires 1 transistors





MEMORY

❖ Register File tradeoffs

- ❑ + Very fast (a few gate delays for both read and write)
- ❑ + Adding extra ports is straightforward
- ❑ – Expensive, doesn't scale
- ❑ – Volatile

❖ Volatile Memory alternatives: SRAM, DRAM, ...

- ❑ – Slower
- ❑ + Cheaper, and scales well
- ❑ – Volatile

❖ Non-Volatile Memory (NV-RAM): Flash, EEPROM, ...

- ❑ + Scales well
- ❑ – Limited lifetime; degrades after 100000 to 1M writes

